

On non-ideal voltage and current measurement tools

Latipov Vladimir && Onishenko Sergiy

26.09.2020

Contents

Contents	1
0.1 Abstract	2
0.2 Experiments	3
0.3 Solving equation system	6
0.4 Measurement Results	7
0.5 The Answer	7


0.1 Abstract

The contents of this section should be too abstract for me to be able to write it.

0.2 Experiments

There were 3 experiments and 4 measurements arranged:


Experiment №1: Sequential plugging in

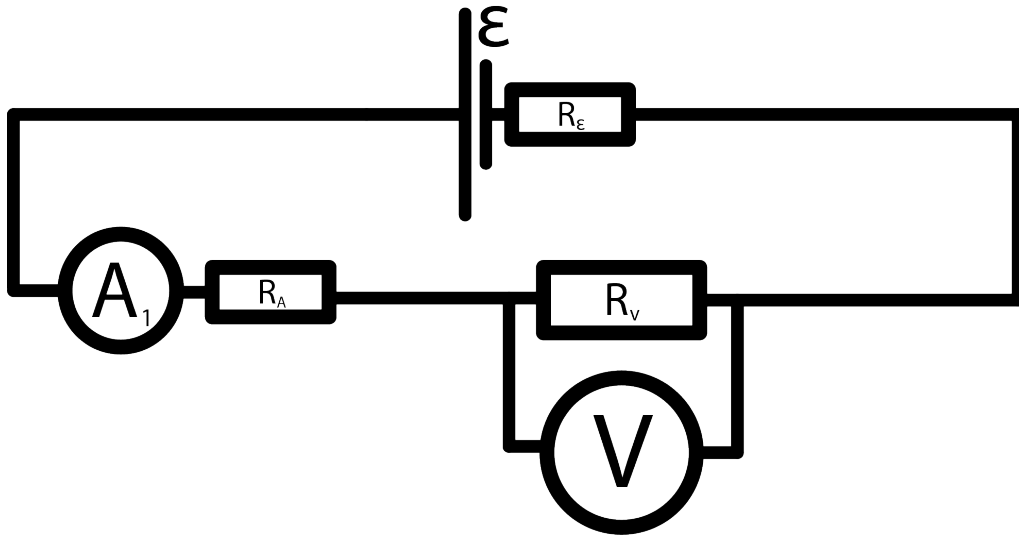


$$A_1 = \frac{\varepsilon}{R_{all}}$$

$$V_1 = \varepsilon \cdot \frac{R_v}{R_{all}}$$

$$R_{all} = R_\varepsilon + R_A + R_v$$

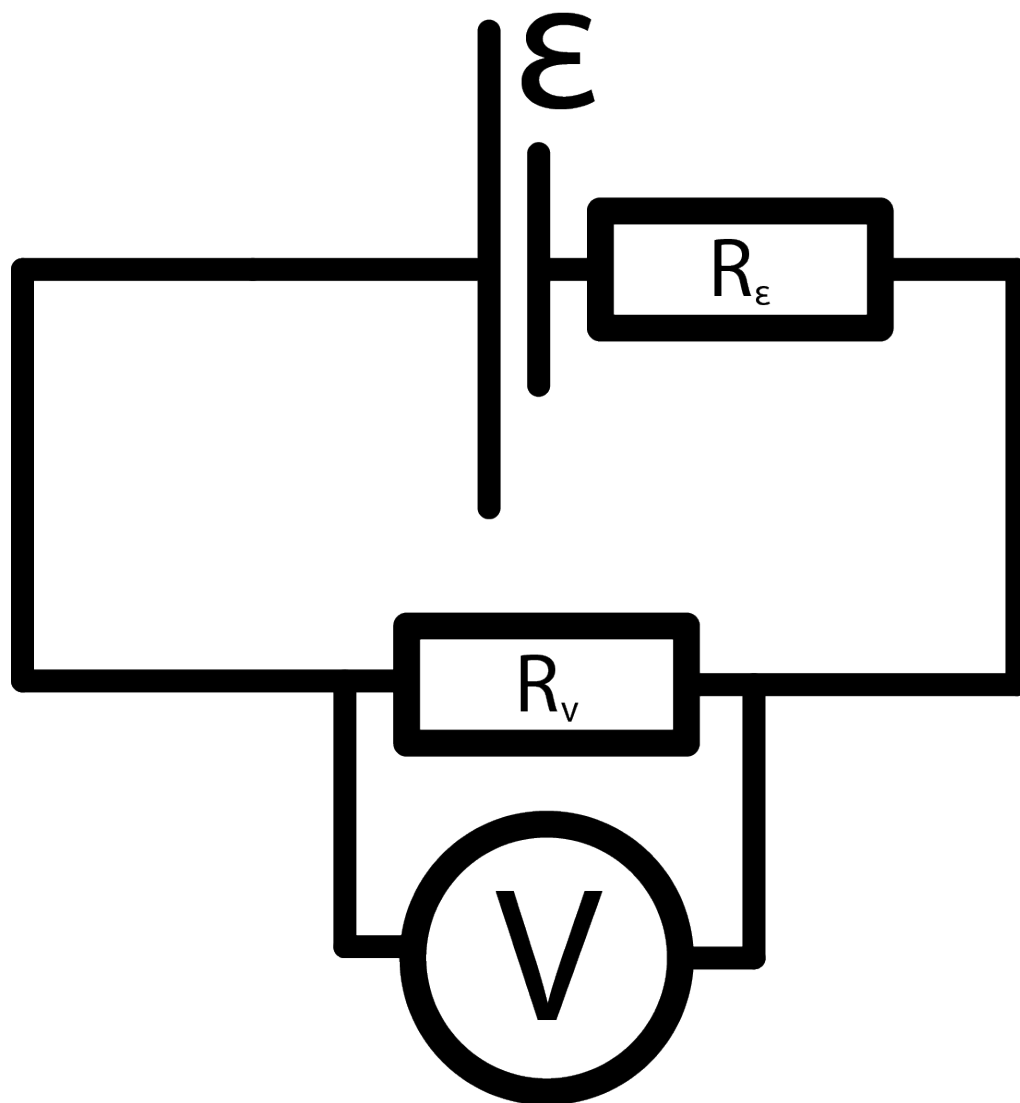Experiment №2: Only Voltmeter

$$V_2 = \varepsilon \cdot \frac{R_v}{R_v + R_\varepsilon}$$

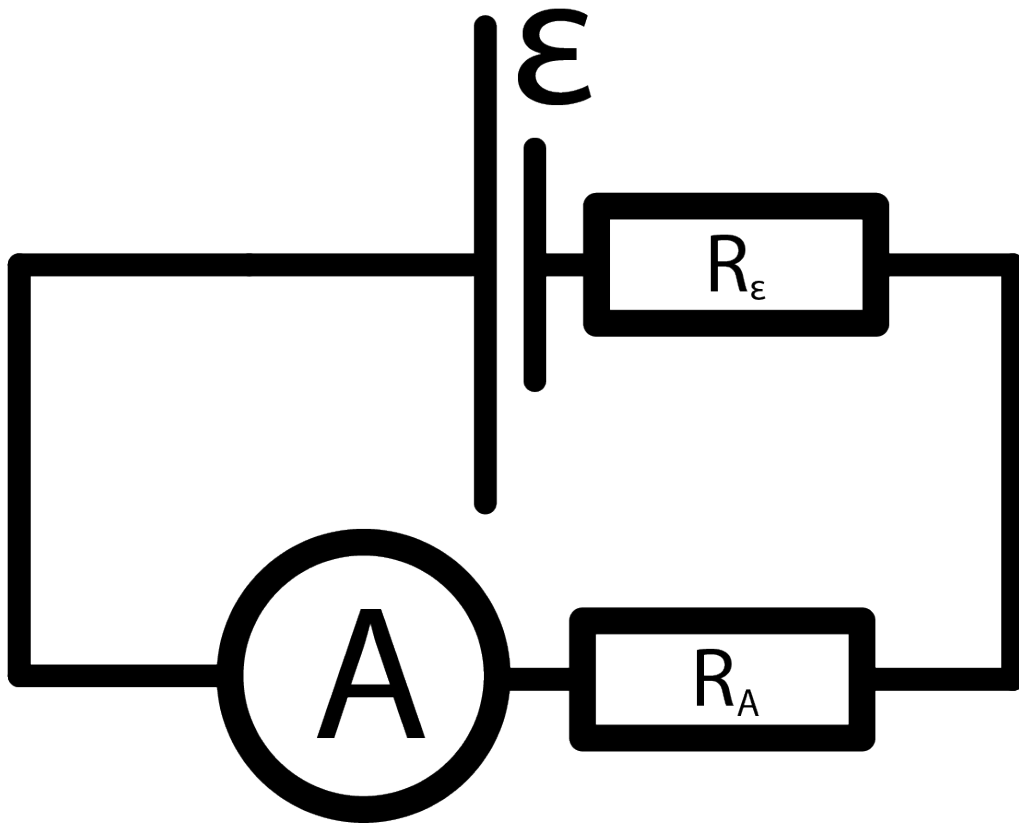Experiment №3: Only Ampermeter

$$A_3 = \varepsilon \cdot \frac{1}{R_A + R_\varepsilon}$$

0.3 Solving equation system

Some bold, italic and underlined text here

$$A_1 = \frac{\varepsilon}{R_{all}} \quad (1)$$

$$V_1 = \varepsilon \cdot \frac{R_v}{R_{all}} \quad (2)$$

$$R_v = \frac{V_1}{A_1}$$

$$V_2 = \varepsilon \cdot \frac{R_v}{R_v + R_\varepsilon} \quad (3)$$

$$\varepsilon = V_2 + V_2 \cdot \frac{R_\varepsilon}{R_v}$$

$$A_3 = \varepsilon \cdot \frac{1}{R_A + R_\varepsilon} = \left(V_2 + V_2 \cdot \frac{R_\varepsilon}{R_v} \right) \cdot \frac{1}{R_A + R_\varepsilon} \quad (4)$$

$$A_3 \cdot R_A + A_3 \cdot R_\varepsilon = V_2 + R_\varepsilon \cdot \frac{V_2}{R_v}$$

$$R_\varepsilon \cdot \left(A_3 - \frac{V_2}{R_v} \right) = V_2 + A_3 \cdot R_A$$

$$R_\varepsilon = \frac{V_2 + A_3 \cdot R_A}{A_3 - \frac{V_2}{R_v}}$$

$$(1) \rightarrow A_1 = \frac{\varepsilon}{R_{all}} = \frac{\varepsilon}{R_v + R_A + R_\varepsilon} = \frac{\varepsilon}{R_v + R_A + \frac{V_2 + A_3 \cdot R_A}{A_3 - \frac{V_2}{R_v}}} = \frac{\varepsilon}{R_v + \frac{V_2}{A_3 - \frac{V_2}{R_v}} + R_A \cdot \left(1 + \frac{A_3}{A_3 - \frac{V_2}{R_v}} \right)}$$

$$\varepsilon = V_2 + V_2 \cdot \frac{\frac{V_2 + A_3 \cdot R_A}{A_3 - \frac{V_2}{R_v}}}{R_v} = V_2 + V_2 \cdot \frac{\frac{V_2}{A_3 - \frac{V_2}{R_v}} + \frac{A_3 \cdot R_A}{A_3 - \frac{V_2}{R_v}}}{R_v} = V_2 + \frac{V_2^2}{R_v \cdot A_3 - V_2} + R_A \cdot \frac{A_3 \cdot V_2}{A_3 \cdot R_v - V_2}$$

$$V_2 + \frac{V_2^2}{R_v \cdot A_3 - V_2} + R_A \cdot \frac{A_3 \cdot V_2}{A_3 \cdot R_v - V_2} = A_1 \cdot R_v + \frac{V_2 \cdot A_1}{A_3 - \frac{V_2}{R_v}} + R_A \cdot A_1 \cdot \left(1 + \frac{A_3}{A_3 - \frac{V_2}{R_v}} \right)$$

$$\begin{aligned}
R_A \cdot \frac{A_3 \cdot V_2}{A_3 \cdot R_v - V_2} - R_A \cdot A_1 \cdot \left(1 + \frac{A_3}{A_3 - \frac{V_2}{R_v}}\right) &= A_1 \cdot R_v + \frac{V_2 \cdot A_1}{A_3 - \frac{V_2}{R_v}} - V_2 - \frac{V_2^2}{R_v \cdot A_3 - V_2} \\
R_A \cdot \left(\frac{A_3 \cdot V_2}{A_3 \cdot R_v - V_2} - A_1 \cdot \left(1 + \frac{A_3}{A_3 - \frac{V_2}{R_v}}\right)\right) &= A_1 \cdot R_v + \frac{V_2 \cdot A_1}{A_3 - \frac{V_2}{R_v}} - V_2 - \frac{V_2^2}{R_v \cdot A_3 - V_2} \\
R_A &= \frac{A_1 \cdot R_v + \frac{V_2 \cdot A_1}{A_3 - \frac{V_2}{R_v}} - V_2 - \frac{V_2^2}{R_v \cdot A_3 - V_2}}{\frac{A_3 \cdot V_2}{A_3 \cdot R_v - V_2} - A_1 \cdot \left(1 + \frac{A_3}{A_3 - \frac{V_2}{R_v}}\right)} \\
R_\varepsilon &= \frac{V_2 + A_3 \cdot R_A}{A_3 - \frac{V_2}{R_v}} \\
\varepsilon &= V_2 + V_2 \cdot \frac{R_\varepsilon}{R_v}
\end{aligned}$$

0.4 Measurement Results

We're neglecting the inaccuracy of the pre-determined upper device measurement limit which is written on those devices. It's inaccuracy is pretty low!

$$\begin{aligned}
A_1 &= ((0.6 \pm 0.07) \text{ Ampere}) \times \frac{15.8}{2000} = (4.7 \pm 0.6) \text{ milliAmpere} \\
V_1 &= ((3.25 \pm 0.1) \text{ Volt}) \times \frac{6.1}{6} = (3.30 \pm 0.1) \text{ Volt} \\
V_2 &= ((3.7 \pm 0.1) \text{ Volt}) \times \frac{6.1}{6} = (3.76 \pm 0.1) \text{ Volt} \\
A_3 &= ((1.8 \pm 0.07) \text{ Ampere}) \times \frac{15.8}{2000} = (14.22 \pm 0.6) \text{ milliAmpere}
\end{aligned}$$

0.5 The Answer

So, the impedance values are the following:

$$R_v = 1 \quad R_e = 1 \quad R_A = 1 \quad \varepsilon = 1$$