

# **On non-ideal voltage and current measurement tools**

Latipov Vladimir && Onishenko Sergiy

26.09.2020

# Contents

<b>1</b>	<b>Abstract</b>	<b>2</b>
<b>2</b>	<b>Experiments</b>	<b>2</b>
2.1	Experiment №1: Sequential plugging in . . . . .	2
2.2	Experiment №2: Only Voltmeter . . . . .	3
2.3	Experiment №3: Only Amperemeter . . . . .	4
<b>3</b>	<b>Solving equation system</b>	<b>4</b>
<b>4</b>	<b>Measurement Results</b>	<b>6</b>
<b>5</b>	<b>The Answer</b>	<b>6</b>


# 1 Abstract

The contents of this section should be too abstract for me to be able to write it.

## 2 Experiments

There were 3 experiments and 4 measurements arranged:
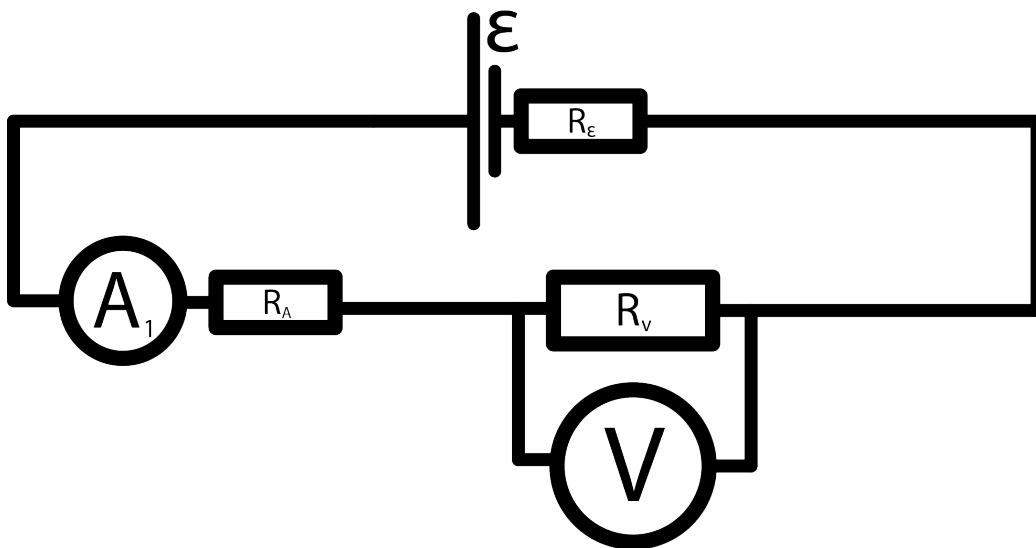
### 2.1 Experiment №1: Sequential plugging in




$$A_1 = \frac{\varepsilon}{R_{all}}$$

$$V_1 = \varepsilon \cdot \frac{R_v}{R_{all}}$$


$$R_{all} = R_{\varepsilon} + R_A + R_v$$

## 2.2 Experiment №2: Only Voltmeter

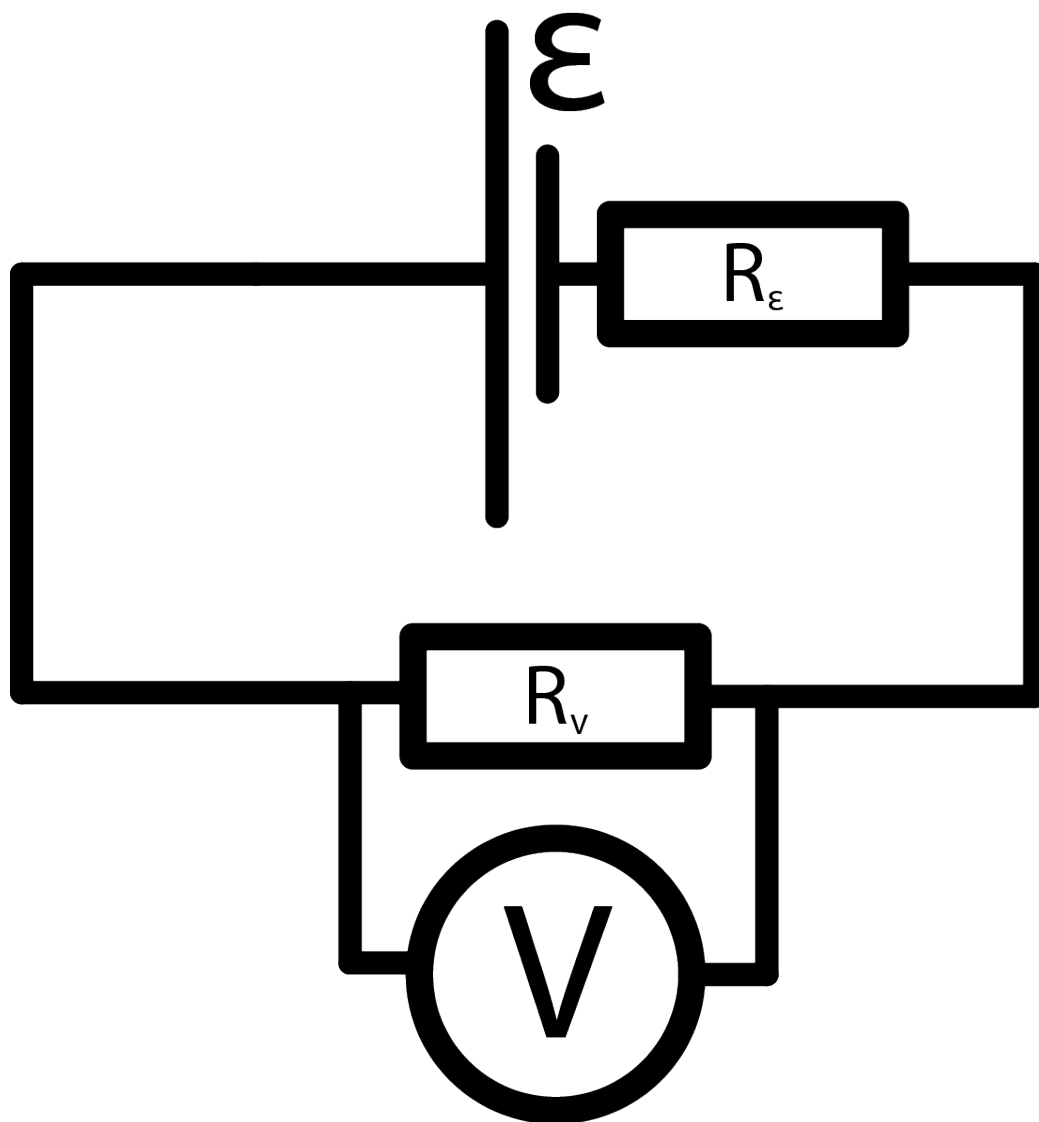

$$V_2 = \varepsilon \cdot \frac{R_v}{R_v + R_\varepsilon}$$

### 2.3 Experiment №3: Only Ampermeter

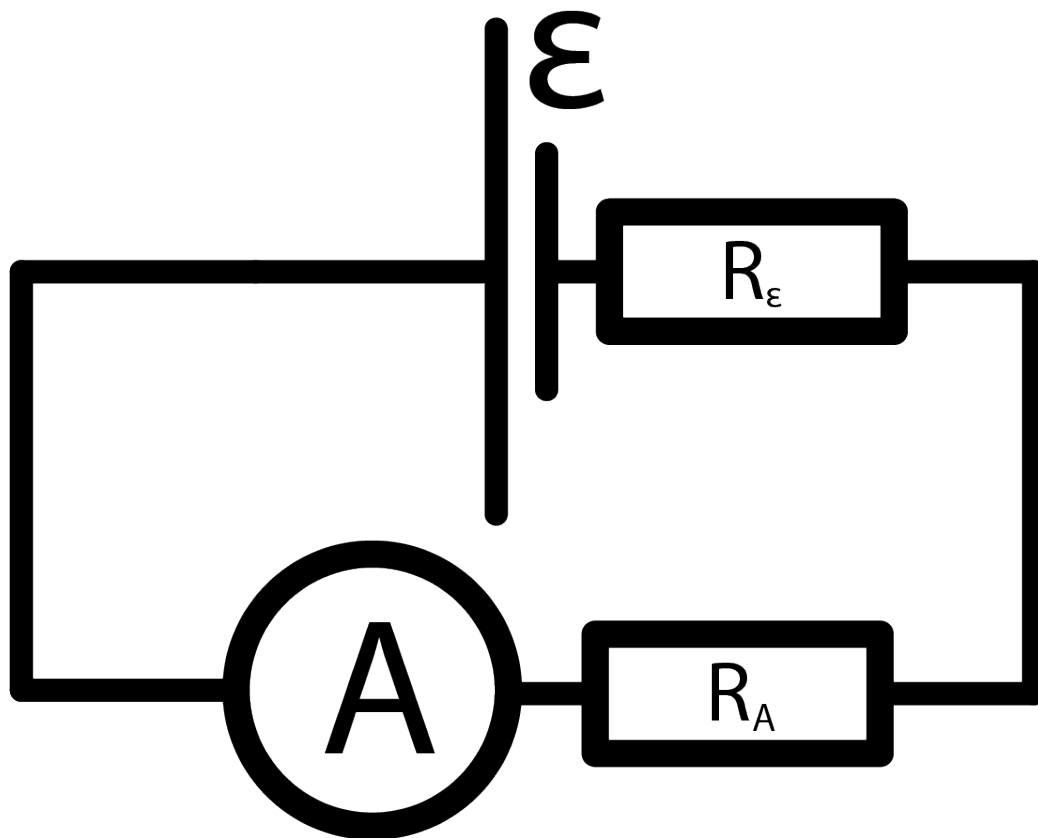

$$A_3 = \varepsilon \cdot \frac{1}{R_A + R_\varepsilon}$$

### 3 Solving equation system

Some bold, italic and underlined text here

$$A_1 = \frac{\varepsilon}{R_{all}} \quad (1)$$

$$V_1 = \varepsilon \cdot \frac{R_v}{R_{all}} \quad (2)$$

$$R_v = \frac{V_1}{A_1}$$

$$V_2 = \varepsilon \cdot \frac{R_v}{R_v + R_\varepsilon} \quad (3)$$

$$\varepsilon = V_2 + V_2 \cdot \frac{R_\varepsilon}{R_v}$$

$$A_3 = \varepsilon \cdot \frac{1}{R_A + R_\varepsilon} = \left( V_2 + V_2 \cdot \frac{R_\varepsilon}{R_v} \right) \cdot \frac{1}{R_A + R_\varepsilon} \quad (4)$$

$$A_3 \cdot R_A + A_3 \cdot R_\varepsilon = V_2 + R_\varepsilon \cdot \frac{V_2}{R_v}$$

$$R_\varepsilon \cdot \left( A_3 - \frac{V_2}{R_v} \right) = V_2 + A_3 \cdot R_A$$

$$R_\varepsilon = \frac{V_2 + A_3 \cdot R_A}{A_3 - \frac{V_2}{R_v}}$$

$$(1) \rightarrow A_1 = \frac{\varepsilon}{R_{all}} = \frac{\varepsilon}{R_v + R_A + R_\varepsilon} = \frac{\varepsilon}{R_v + R_A + \frac{V_2 + A_3 \cdot R_A}{A_3 - \frac{V_2}{R_v}}} = \frac{\varepsilon}{R_v + \frac{V_2}{A_3 - \frac{V_2}{R_v}} + R_A \cdot \left( 1 + \frac{A_3 \cdot V_2}{A_3 - \frac{V_2}{R_v}} \right)}$$

$$\varepsilon = V_2 + V_2 \cdot \frac{\frac{V_2 + A_3 \cdot R_A}{A_3 - \frac{V_2}{R_v}}}{R_v} = V_2 + V_2 \cdot \frac{\frac{V_2}{A_3 - \frac{V_2}{R_v}} + \frac{A_3 \cdot R_A}{A_3 - \frac{V_2}{R_v}}}{R_v} = V_2 + \frac{V_2^2}{R_v \cdot A_3 - V_2} + R_A \cdot \frac{A_3 \cdot V_2}{A_3 \cdot R_v - V_2}$$

$$V_2 + \frac{V_2^2}{R_v \cdot A_3 - V_2} + R_A \cdot \frac{A_3 \cdot V_2}{A_3 \cdot R_v - V_2} = A_1 \cdot R_v + \frac{V_2 \cdot A_1}{A_3 - \frac{V_2}{R_v}} + R_A \cdot A_1 \cdot \left( 1 + \frac{A_3}{A_3 - \frac{V_2}{R_v}} \right)$$

$$R_A \cdot \frac{A_3 \cdot V_2}{A_3 \cdot R_v - V_2} - R_A \cdot A_1 \cdot \left(1 + \frac{A_3}{A_3 - \frac{V_2}{R_v}}\right) = A_1 \cdot R_v + \frac{V_2 \cdot A_1}{A_3 - \frac{V_2}{R_v}} - V_2 - \frac{V_2^2}{R_v \cdot A_3 - V_2}$$

$$R_A \cdot \left( \frac{A_3 \cdot V_2}{A_3 \cdot R_v - V_2} - A_1 \cdot \left(1 + \frac{A_3}{A_3 - \frac{V_2}{R_v}}\right) \right) = A_1 \cdot R_v + \frac{V_2 \cdot A_1}{A_3 - \frac{V_2}{R_v}} - V_2 - \frac{V_2^2}{R_v \cdot A_3 - V_2}$$

$$R_A = \frac{A_1 \cdot R_v + \frac{V_2 \cdot A_1}{A_3 - \frac{V_2}{R_v}} - V_2 - \frac{V_2^2}{R_v \cdot A_3 - V_2}}{\frac{A_3 \cdot V_2}{A_3 \cdot R_v - V_2} - A_1 \cdot \left(1 + \frac{A_3}{A_3 - \frac{V_2}{R_v}}\right)}$$

$$R_\varepsilon = \frac{V_2 + A_3 \cdot R_A}{A_3 - \frac{V_2}{R_v}}$$

$$\varepsilon = V_2 + V_2 \cdot \frac{R_\varepsilon}{R_v}$$

## 4 Measurement Results

We're neglecting the inaccuracy of the pre-determined upper device measurement limit which is written on those devices. It's inaccuracy is pretty low!

$$A_1 = ((0.6 \pm 0.07) \text{ Ampere}) \times \frac{15.8}{2000} = (4.7 \pm 0.6) \text{ milliAmpere}$$

$$V_1 = ((3.25 \pm 0.1) \text{ Volt}) \times \frac{6.1}{6} = (3.30 \pm 0.1) \text{ Volt}$$

$$V_2 = ((3.7 \pm 0.1) \text{ Volt}) \times \frac{6.1}{6} = (3.76 \pm 0.1) \text{ Volt}$$

$$A_3 = ((1.8 \pm 0.07) \text{ Ampere}) \times \frac{15.8}{2000} = (14.22 \pm 0.6) \text{ milliAmpere}$$

## 5 The Answer

So, the impedance values are the following:

$$R_v = 1 \quad R_e = 1 \quad R_A = 1 \quad \varepsilon = 1$$