

On non-ideal voltage and current measurement tools

Latipov Vladimir && Onishenko Sergiy

26.09.2020

Contents

1	Abstract	2
2	Experiments	2
2.1	Experiment №1: Sequential plugging in	2
2.2	Experiment №2: Only Voltmeter	3
2.3	Experiment №3: Only Amperemeter	4
3	Solving equation system	4
4	The Answer	6

1 Abstract

It's contents should be too abstract for me to be able to write it.

2 Experiments

There were 4 experiments arranged:

2.1 Experiment №1: Sequential plugging in



2.2 Experiment №2: Only Voltmeter



2.3 Experiment №3: Only Ampermeter



3 Solving equation system

Some bold, italic and underlined text here

$$A_1 = \frac{\varepsilon}{R_{all}} \quad (1)$$

$$V_1 = \varepsilon \cdot \frac{R_v}{R_{all}} \quad (2)$$

$$R_v = \frac{V_1}{A_1}$$

$$V_2 = \varepsilon \cdot \frac{R_v}{R_v + R_\varepsilon} \quad (3)$$

$$\varepsilon = V_2 + V_2 \cdot \frac{R_\varepsilon}{R_v}$$

$$A_3 = \varepsilon \cdot \frac{1}{R_A + R_\varepsilon} = \left(V_2 + V_2 \cdot \frac{R_\varepsilon}{R_v} \right) \cdot \frac{1}{R_A + R_\varepsilon} \quad (4)$$

$$A_3 \cdot R_A + A_3 \cdot R_\varepsilon = V_2 + R_\varepsilon \cdot \frac{V_2}{R_v}$$

$$R_\varepsilon \cdot \left(A_3 - \frac{V_2}{R_v} \right) = V_2 + A_3 \cdot R_A$$

$$R_\varepsilon = \frac{V_2 + A_3 \cdot R_A}{A_3 - \frac{V_2}{R_v}}$$

$$(1) \rightarrow A_1 = \frac{\varepsilon}{R_{all}} = \frac{\varepsilon}{R_v + R_A + R_\varepsilon} = \frac{\varepsilon}{R_v + R_A + \frac{V_2 + A_3 \cdot R_A}{A_3 - \frac{V_2}{R_v}}} = \frac{\varepsilon}{R_v + \frac{V_2}{A_3 - \frac{V_2}{R_v}} + R_A \cdot \left(1 + \frac{A_3}{A_3 - \frac{V_2}{R_v}} \right)}$$

$$\varepsilon = V_2 + V_2 \cdot \frac{\frac{V_2 + A_3 \cdot R_A}{A_3 - \frac{V_2}{R_v}}}{R_v} = V_2 + V_2 \cdot \frac{\frac{V_2}{A_3 - \frac{V_2}{R_v}} + \frac{A_3 \cdot R_A}{A_3 - \frac{V_2}{R_v}}}{R_v} = V_2 + \frac{V_2^2}{R_v \cdot A_3 - V_2} + R_A \cdot \frac{A_3 \cdot V_2}{A_3 \cdot R_v - V_2}$$

$$V_2 + \frac{V_2^2}{R_v \cdot A_3 - V_2} + R_A \cdot \frac{A_3 \cdot V_2}{A_3 \cdot R_v - V_2} = A_1 \cdot R_v + \frac{V_2 \cdot A_1}{A_3 - \frac{V_2}{R_v}} + R_A \cdot A_1 \cdot \left(1 + \frac{A_3}{A_3 - \frac{V_2}{R_v}}\right)$$

$$R_A \cdot \frac{A_3 \cdot V_2}{A_3 \cdot R_v - V_2} - R_A \cdot A_1 \cdot \left(1 + \frac{A_3}{A_3 - \frac{V_2}{R_v}}\right) = A_1 \cdot R_v + \frac{V_2 \cdot A_1}{A_3 - \frac{V_2}{R_v}} - V_2 - \frac{V_2^2}{R_v \cdot A_3 - V_2}$$

$$R_A \cdot \left(\frac{A_3 \cdot V_2}{A_3 \cdot R_v - V_2} - A_1 \cdot \left(1 + \frac{A_3}{A_3 - \frac{V_2}{R_v}}\right) \right) = A_1 \cdot R_v + \frac{V_2 \cdot A_1}{A_3 - \frac{V_2}{R_v}} - V_2 - \frac{V_2^2}{R_v \cdot A_3 - V_2}$$

$$R_A = \frac{A_1 \cdot R_v + \frac{V_2 \cdot A_1}{A_3 - \frac{V_2}{R_v}} - V_2 - \frac{V_2^2}{R_v \cdot A_3 - V_2}}{\frac{A_3 \cdot V_2}{A_3 \cdot R_v - V_2} - A_1 \cdot \left(1 + \frac{A_3}{A_3 - \frac{V_2}{R_v}}\right)}$$

4 The Answer

So, the impedance values are the following:

$$R_v = 1 \quad R_e = 1 \quad R_A = 1 \quad \varepsilon = 1$$